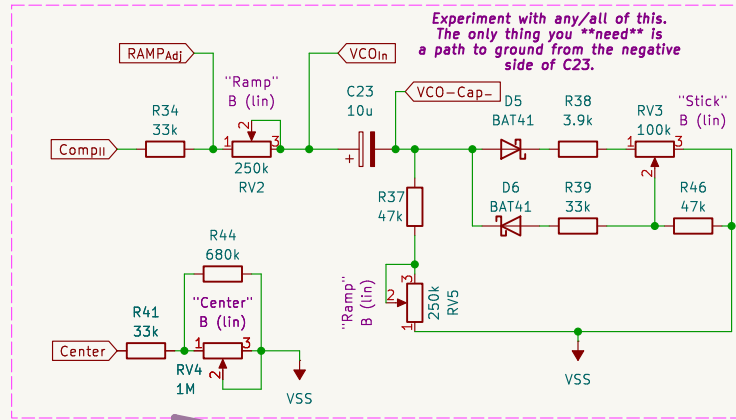


2. PLL + Control

- 470n = more rumble/glitch (less "charge up" after silence)
 - 150nF - 330n = between 470nF and 100nF...
 - 22nF-100nF = crisper highs, less rumbley lows
 - 10nF or less = more nasal + gets static

Omit entirely for cleanest tracking!
 (But also less sustain)
 My current preference is 100nF
 It's 470nF in the video

Experiment with any/all of this.
 The only thing you ****need**** is
 a path to ground from the negative
 side of C23.



4. Auto-Adj

The diagram illustrates the internal structure of the LM311, showing the connection of its pins to the VDD and VSS rails. The LM311 is represented by a triangle with pins 1 through 8. Pin 1 is connected to VSS. Pin 2 is connected to RAMPAdj. Pin 3 is connected to VCOIn. Pin 4 is connected to VSS. Pin 5 is connected to VSS. Pin 6 is connected to VSS. Pin 7 is connected to VCO-Cap-. Pin 8 is connected to VDD. A 100nF capacitor (C26) is connected between VDD and VSS. A 1k resistor (R47) is connected between VDD and VSS. The output of the LM311 is connected to VDD. The diagram is labeled with 'U5 LM311' and 'VDD', 'VSS', 'RAMPAdj', 'VCOIn', 'VCO-Cap-', 'C26 100n', 'R47 1k'.

3. Suboctaves

The circuit diagram illustrates the generation of suboctaves. It consists of two main stages, each using a 4013 monostable multivibrator (labeled U2A and U2B) to generate a square wave pulse. The first stage (U2A) is triggered by the VCOOut signal through a 10k resistor (R15) and a 680pF capacitor (C13). The output of U2A (Q) is connected to a 10k resistor (R16) and a 1N914 diode (D4) to ground (GND). The second stage (U2B) is triggered by the output of U2A (Q) through a 33k resistor (R17). The output of U2B (Q) is connected to a 10k resistor (R18) and a 1N914 diode (D4) to ground (GND). The outputs of both stages are connected to a common point, which is then connected to a 47k resistor (R45) and a 47k resistor (R42) to ground (GND). The final output is labeled SubOctaves.

1. Input + Boost

Doesn't have to be exact. "Big" is fine.
We just wanna make sure we smush the
signal a bunch and cut off the high-highs.

(Any common op amp is probably fine)

Boosted

PLL Notes:

1. RV4 + RV2 make noise when:
both up/down/full-opposite.
(Only one extreme == usable).
Play with sizes/ranges!
2. RV4 and C12 set the center frequency:
If R4 gets smaller; make C12 bigger.
3. Increase R37 = less droop/slide/wah.
4. Fiddle with the diodes and stuff!
5. P.S. Signals ARE also at PC1/PCP, BTW.
6. When PCP = HIGH + PC1 = LOW 4+ times
in a row: you are at frequency lock!
7. If you put a counter/divider between
CompII out and VCOIn, the PLL will
shift the frequency UP as much as the
divider divides. Use one half of the
CD4013 in the loop instead: octave up!

4. Summing Stage & Output

SW1
Sub-Octaves

SubOctaves

VCOBuff

R20 62k

R23 47k

R24 200k

R26 10k

C22 10u

R32 10k

100k RV1

R31 200k

R33 2.2k

R35 20k

R36 2.2k

Output J3

GNDA

GNDS

4558 U4A

4558 U4B

VCOOut

R13 200k

R14 100k

C19 470p

R40 10k

R25 24k

Volume B (lin)

For insulated jacks, DO attach ground wire and attach at R21.

Metal jacks + enclosure: do NOT solder wire to sleeve. (Grounded through enclosure)

0. Power + VRef

Or any Schottky.
Or any Diode at all that is rated for:

- * 180mA+ repetitive forward current
- * 80mA+ continuous forward current
- * rated for 500mW
- * 24V continuous reverse voltage

(All overestimates)

This is the "star point"
for all of the CD4xxx IC's

This is the "star point"
for all your 0V grounds!

"Analog Ground"
a.k.a. "Audio Ground"
a.k.a. "Ground Reference"

"DC Ground"
a.k.a. "Supply Ground"

VCC
R2 33k
R3 33k
GND A
GND B

GND A
C2 10u
C3 100n
GND B


VCC
R1 100
C1 100u
GND A
GND B

VDD
R19 100
C14 100u
VSS
D1 BAT43
J1 DC-In
1
2
GND

VCC
C17 100n
U3C TL072
V+
V-
GND A

VCC
C16 100n
U4C 4558
V+
V-
GND A

VDD
C15 100n
U2C 4013
VDD
VSS
VSS

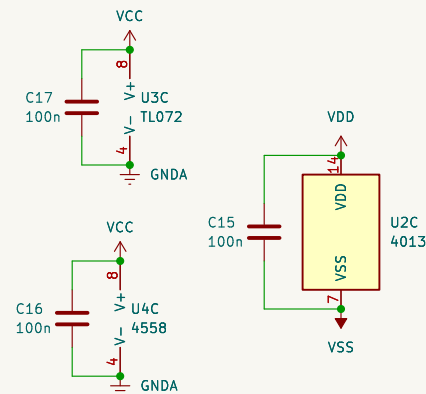

WARNINGS :

- LUNCHTIME HACK / ALPHA!
- Keep the volume low while experimenting. This circuit can produce very high or loud tones if adjusted live!
- Breadboard before you solder anything! This is hastily documented and NOT double checked! (Yet)

- Connect ground symbols at respective star grounds
- You can omit VSS and just use GND as audio ground (I think the signal will swamp out any noise anyway)
- Octave down is optional: just exclude CD4013
- This was another lunch hack: don't judge.
- Do hack!

WARNING: HACK! NOT CHECKED FOR ERRORS (yet).
Pink Circles = Fiddle with these! (Fiddle with any)
Andrew T. Canaday (povins), D.B. Buchholz (QuickButterfly_4571)
Sheet: /
File: OSM2.kicad_sch

Title: Olangrall's Sex Machine (II)

Size: B	Date: 2025-01-18
---------	------------------

KiCad E.D.A. 8.0.7

Rev: 0.1.0a

id: 1/1